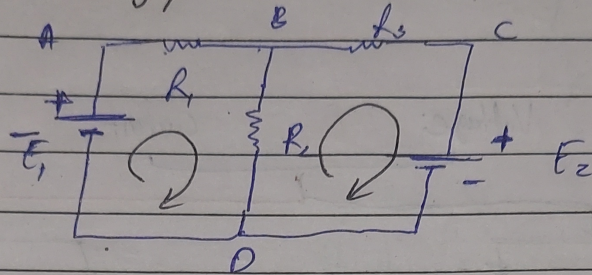


Unit - 2 DC circuit

* Network Terminology:-



(i) Active elements:-

Those elements in the network which supplies energy to the circuit, E_1 and E_2 are active elements.

(ii) Passive elements:-

Which consumes energy or receive energy to the circuit is called pass.

(iii) Node:- A point in a network where two or more elements join. $\{A, B, C, D\}$ are nodes

(iv) Junction:- A point in a network where 3 or more elements join. (B and D)


(v) loop :- The closed path of a network.
 ΔABD $\Delta ABCD$ ΔBCD

* Mesh:- The most elementary form of a loop that can't be further divided.

ΔABD ΔBCD


★ **Branch** :- The path of a network which lies between two junction points.

★ **Sources** :-

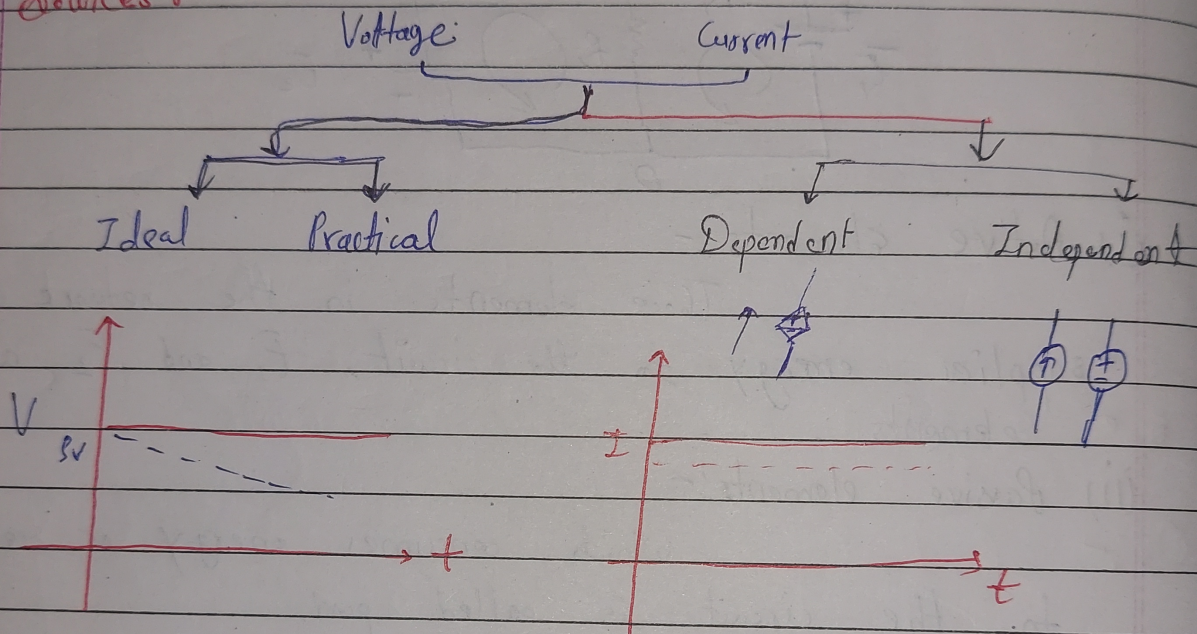


• **Voltage Depen. Voltage Source** :-
(VDVS)

- CDVS
- VDVS
- CDCS

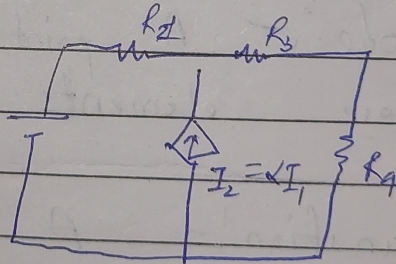


Source Transformation :-

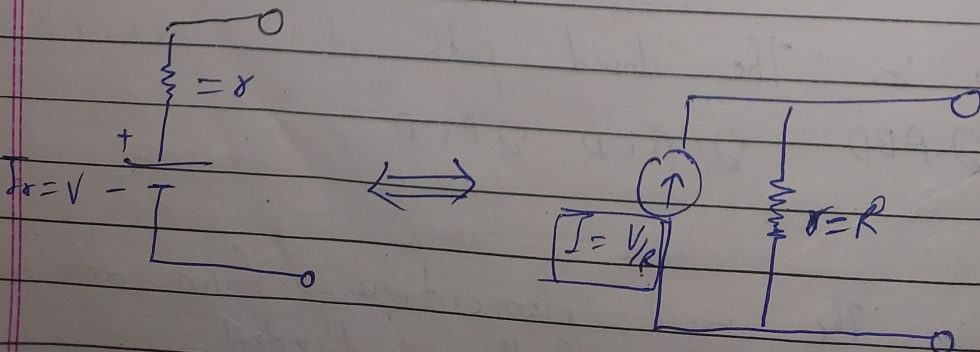


* Kirchoff's law :-

(i)

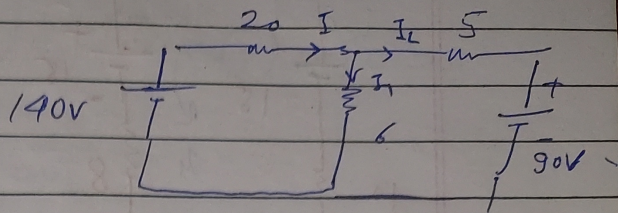


find I and P in 6Ω resistance.

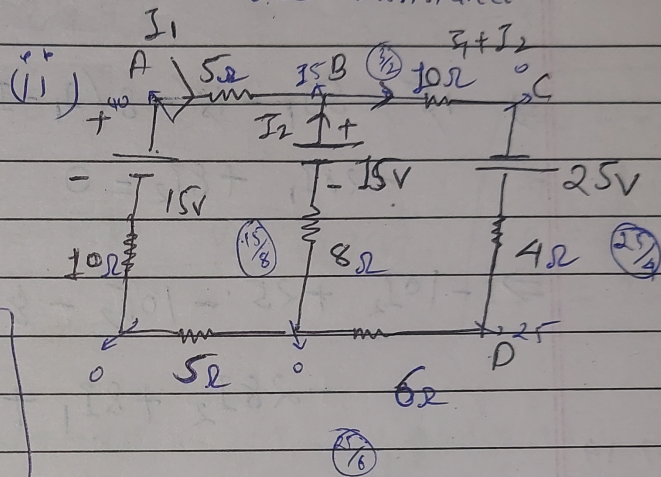

$$\begin{aligned} I_1 &= 0.44 \\ I_2 &= 1.11 \\ I_1 + I_2 &= 1.55 \end{aligned}$$

* Mesh Analysis :-

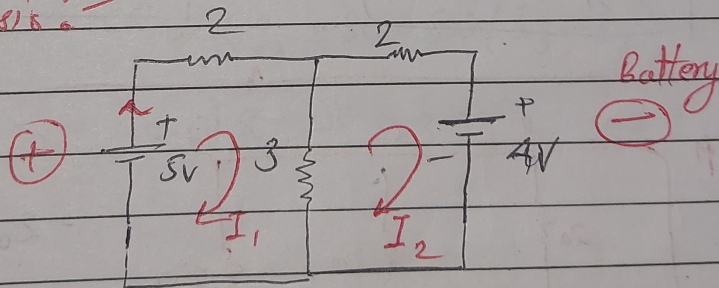

$$\Rightarrow 5 - 2I_1 - 3(I_1 - I_2) = 0 \Rightarrow -2I_2 - 4 - 3(I_2 - I_1) = 0$$


$$\Rightarrow 5 - 2I_1 - 3I_1 + 3I_2 = 0 \Rightarrow -2I_2 - 4 - 3I_2 + 3I_1 = 0$$

$$\Rightarrow (5 - 5I_1 + 3I_2 = 0)$$

$$(-4 + 3I_1 + 5I_2 = 0)$$

$$I_1 = \frac{+39}{40}$$

$$I_2 = \frac{-15}{40}$$

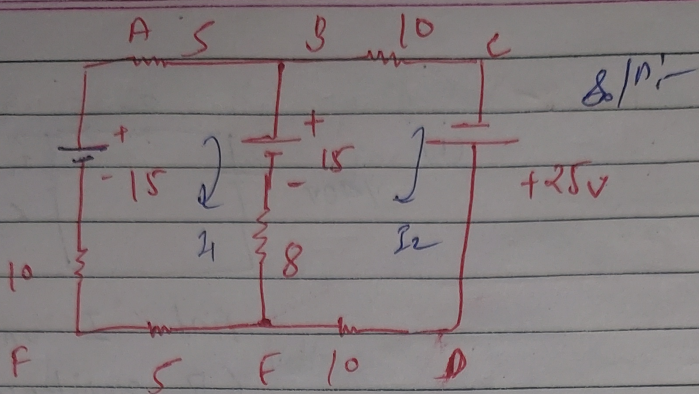

$$\Rightarrow 15 - 5I_1 - 15 - 8(I_1 - I_2) - 5I_1 + 10I_1 = 0$$

$$-28I_1 + 8I_2 = 0 \quad 8I_2 = 28I_1$$

$$\Rightarrow -10I_2 + 25 - 10I_2 - 8(I_2 - I_1) + 15 = 0$$

$$-28I_2 + 8I_1 + 40 = 0$$


$14 \times 7 = 14$
 ~~$28 \times 28 I_1$~~
 $\frac{8}{4}$

$$-14 \times 7 = I_1$$

$$\frac{14 \times 7 \times 28}{8} = I_2$$

$$I_1 = 0.44 \text{ A}$$

$$I_2 = 1.54 \text{ A}$$

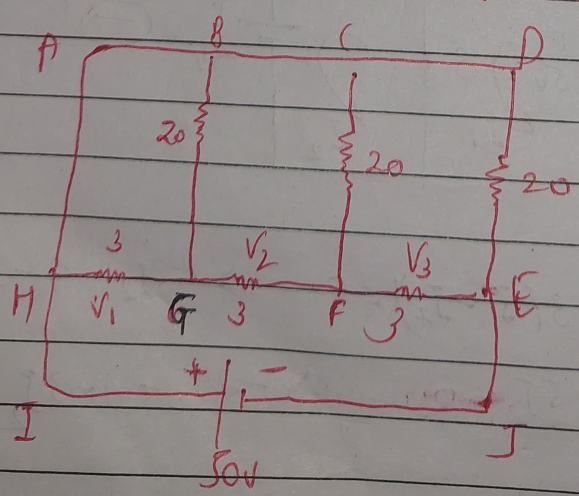

$$-20(I_1 - I_2)$$

$$-3(I_1 - I_4) = 0$$

$$-20(I_2 - I_3)$$

$$-20(I_2 - I_3)$$

$$-3(I_3 - I_4)$$

$$\Rightarrow -20I_3 - 3(I_3 - I_4) - 20(I_3 - I_2) = 0$$

$$-3(I_4 - I_1) - 3(I_4 - I_2) - 3(I_4 - I_3) + 50 = 0$$

$$-23I_1 + 20I_2 + 3I_4 = 0$$

$$+20I_1 - 43I_2 + 20I_3 + 3I_4 = 0$$

1-2
2-3

$$20I_2 - 43I_3 + 3I_4 = 0$$

4-3

$$3I_1 + 3I_2 + 3I_3 - 9I_4 + 50 = 0$$


$$I_3 = 2.5$$

$$I_1 = 4.6$$

$$I_2 = 4.$$

$$I_4 = 9.27A$$
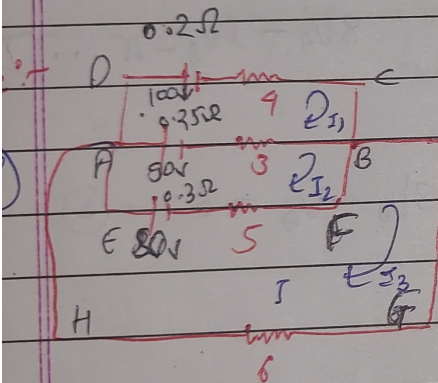
$$V_1 = 13.82V \quad V_2 = 15.83 \quad V_3 = 20.35V$$



$$\textcircled{1} \quad -100 - 4.2I_1 - 3(I_1 - I_2) + 90 = 0$$


$$\textcircled{2} \quad -90 - 3(I_2 - I_1) - (5.0)I_2 + 80 = 0$$

$$\textcircled{3} \quad -6I_3 - 80 - 5.3(I_3 - I_2) = 0$$

$$-11.3I_3 + 5.3I_2 = 80 = 0$$

$I_1 = 6.21$
$I_2 = 11.16$
$I_3 = 12.31$
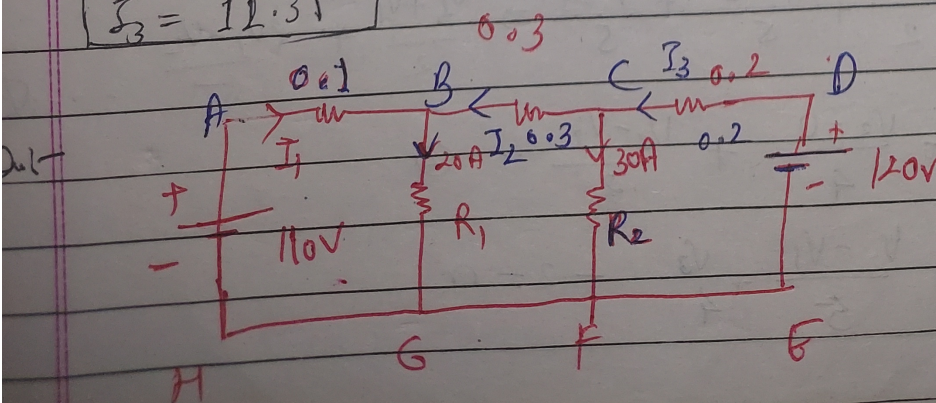
$$I_1 \quad 3\Omega \quad (4.95) \quad (I_2 - I_1)$$



$$R_1 \rightarrow 5.95 \Omega$$


$$R_2 \rightarrow 3.73 \Omega$$

$$I_1 \rightarrow 10A$$

$$I_2 = 10A$$

$$I_3 = 40A$$

Nodal Analysis:-

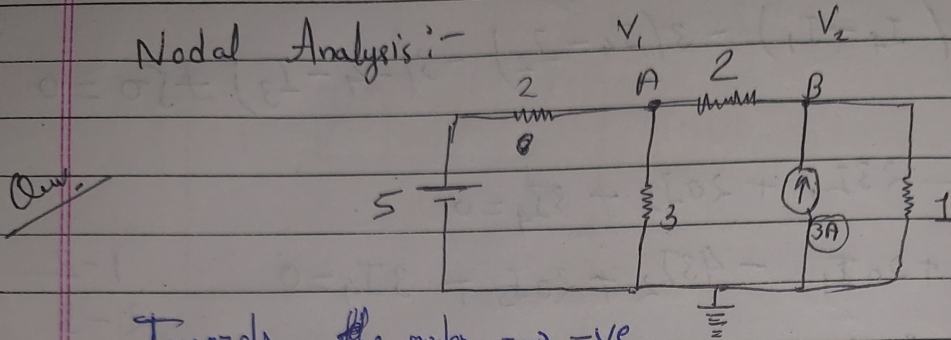

Towards the nodes \Rightarrow -ve
Always from node \rightarrow +ve

• KCL at node A

$$\frac{V_A - 5}{2} + \frac{V_A - 0}{3} + \frac{V_A - V_B}{2} = 0$$


$$3V_A - 15 + 2V_A + 3V_A - 3V_B = 0$$

$$8V_A - 3V_B - 15 = 0 \quad \text{--- (1)}$$

• KCL at node B

$$\frac{V_B - V_A}{2} + \frac{V_B - 0}{1} - 3 = 0 \Rightarrow 3V_B - V_A = 6 \quad \text{--- (2)}$$

Solⁿ:- $V_A = 3$ $V_B = 3$

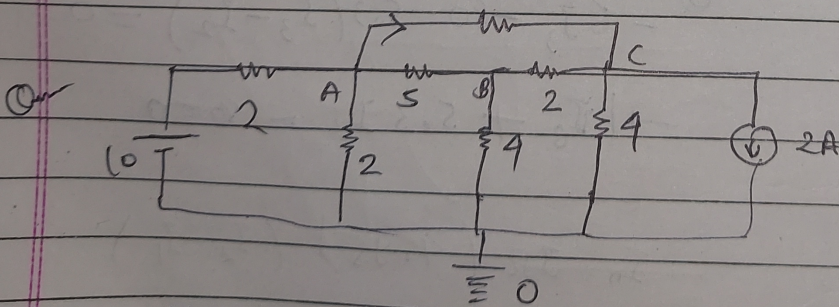

$$\frac{V_A - 10}{2} + \frac{V_A - 0}{2} + \frac{V_A - V_2}{5} + \frac{V_A - V_3}{5} = 0 \Rightarrow \frac{V_1 + V_1}{2} + \frac{2V_1 - V_2}{5} \dots \text{--- (1)}$$

$$\frac{V_2 - V_1}{5} + \frac{V_2 - 0}{4} + \frac{V_2 - V_3}{2} = 0 \quad \text{--- (2)}$$

$$\frac{V_2 - V_2}{4} + \frac{V_2 - V_3}{5} + \frac{V_3}{4} + 2 = 0$$

$$\frac{4V_2 - 4V_1 + 5V_2 + 10(V_2 - V_3)}{20}$$

$$V_A = 3.36 \quad V_B = -0.086, \quad V_C = -1.416$$

~~Norton~~ Network Theorem :-

Theremin's theorem :-

Any 2 terminal of an electrical networks consistence of active elements can be replaced by an equivalent voltage source and equivalence.


The voltage source :- The open circuit voltage btwn the terminal caused by the active network.

$$I_1 = \frac{V_{th}}{R_{th} + R_L}$$


DATE _____
PAGE _____

Unit - 2


DC circuit.

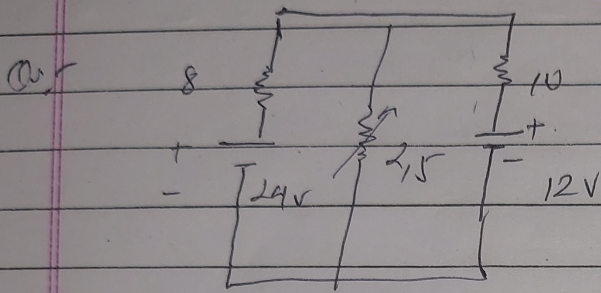

Q2

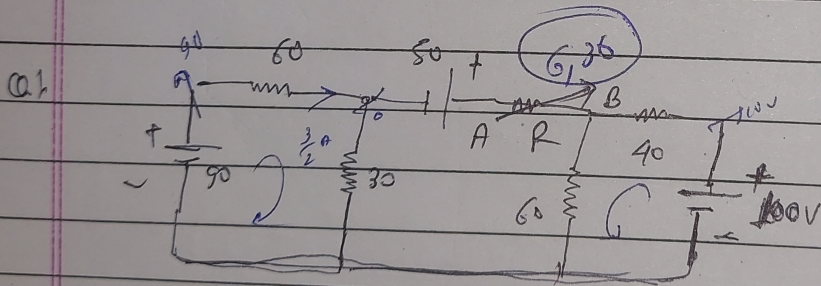

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

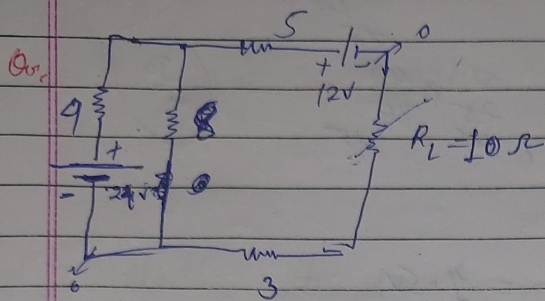

80) ...


$$2A - \frac{4}{10}(I_1 + I_2) - 8(I_1) = 0$$

$$-5I_2 + 12 - I_2(10) = 0$$


$$V_{Th} = 0 + (6 + 0) - 12 = 0 = 4V$$

$$R_{Th} = 10 \cdot 67$$

$$5 + 3 + (4 \parallel 10)$$

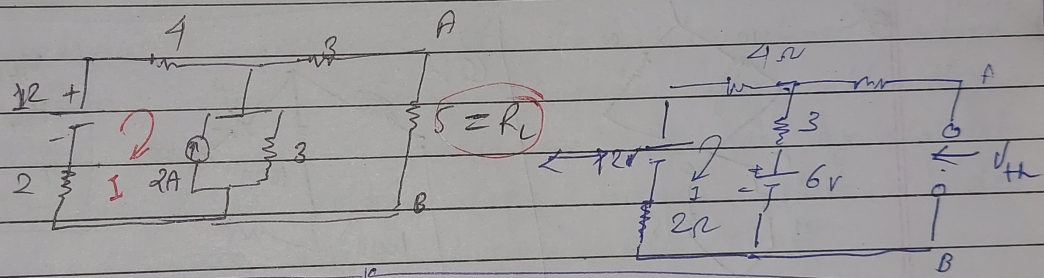

find
 V_{BC}
 V_{AC}

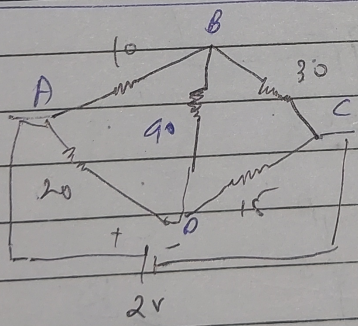

$$\begin{bmatrix} 40 \\ 35 \end{bmatrix}$$

$$R \Rightarrow \frac{56}{3}$$

$$V = \frac{2 \times 3}{58 \cdot 28}$$

$$\frac{3}{28} = I_1 = \frac{30}{28} \times \frac{40}{75} \times \frac{2}{40} = \frac{2}{20}$$

$$V_{Th} =$$

$$I_2 = \frac{3}{28} \times \frac{25}{75} = \frac{2}{35}$$

$$V_1 = 2 \times \frac{40}{75}$$

$$V_2 = 2 \times \frac{35}{75}$$

$$V_{oc} = 30 \times \frac{15 \times 40}{25 \times 25} = \frac{30}{7}$$



$$= 30 \times \frac{1}{7}$$

$$= \frac{30 \times V}{40} = 1.5V$$


$$V_{pc} = 15 I_2 = \frac{15 \times V_2}{35} = 0.857V$$

$$V_{BD} = V_p - V_o = V_{th} = 1.5 - 0.857$$


$$= 0.642V$$

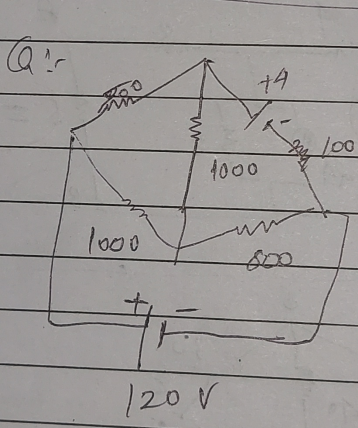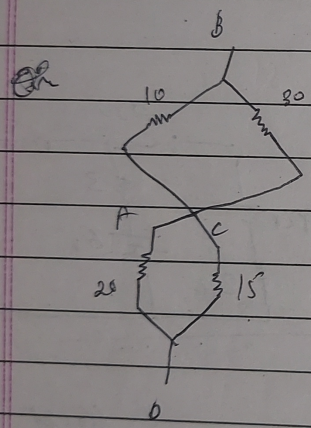

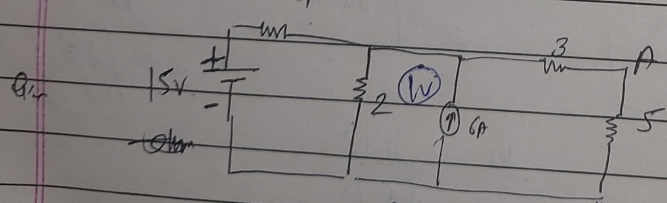$V_{th} = 0.642V$
 $R_{th} = 500 \Omega$
 $I = 1.5mA$



$$= \frac{15}{28}$$

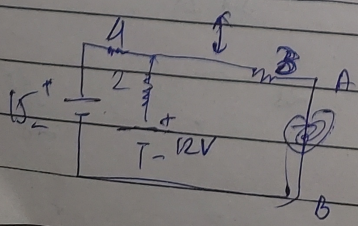

$$3 - 6I = 0$$

$$0.5 = I$$

$$V_{th} = 13$$

$$R_{th} = 4.33$$

$$R_{th} = 3 + (4 \parallel 2)$$


500
100
200
800

$\frac{14}{3} \times 2$
 $\frac{20}{3}$
 $\frac{14}{3}$


$I_L = 1.39 A$

$I = \frac{V_{TH}}{R_{TH} + R_L}$

Norton's theorem :- Any terminal network consisting of voltage sources and resistances can be converted a constant source and a parallel resistance. The magnitude of constant current is equal to the current which will flow when two terminals are short circuited and parallel resistance is the equivalent resistance of the whole network ^{viewed} ~~whipe~~ from open circuited terminals after all the voltage and current source are replaced by the int resistance or voltage source becomes short circuited and current source become open circuit.

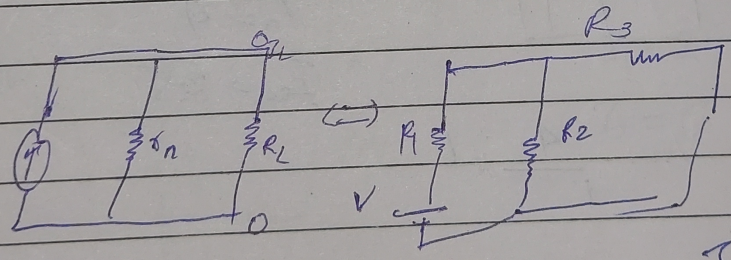

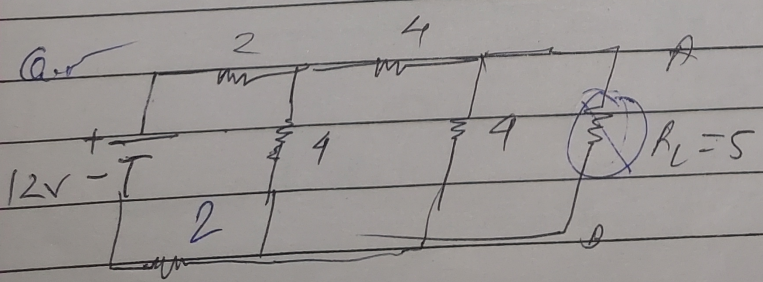$I_L = \frac{V_N \times I_{sc}}{R_N + R_L}$



$I_{sc} = 1 A$

Eliminate R_L


$I = \frac{12}{2+8+2} = 1 A$

$I_N = 2.4$ (By removing battery)

$\frac{2.4}{2+5} \times 1 = I_L$

$\frac{2.4}{7.5}$
 $\frac{2.4}{7.5} \times 1$

Ques

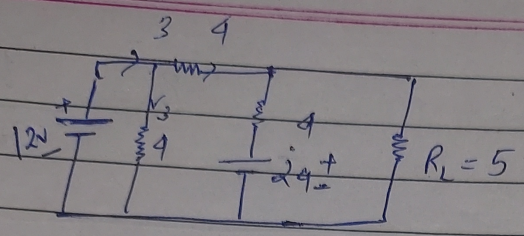


$$I_L = \frac{2}{2+8} \times 9$$

$$I_L = \frac{24}{4} = 6 + 3 = 9 \text{ A}$$

$$r_0 = 2$$

$$\begin{aligned} &= \frac{2 \times 9}{7} \\ &\Rightarrow \frac{18}{7} = 2.55 \end{aligned}$$

Ques 2

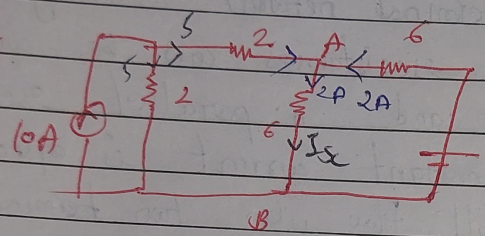


$$I_L = \frac{2 \times 9}{2.4 + 7}$$

$$I_L = \frac{12}{6} = 2 \text{ A}$$

$$I_L = \frac{2.4 \times 7}{8.4} = 2 \text{ A}$$

Ques 3

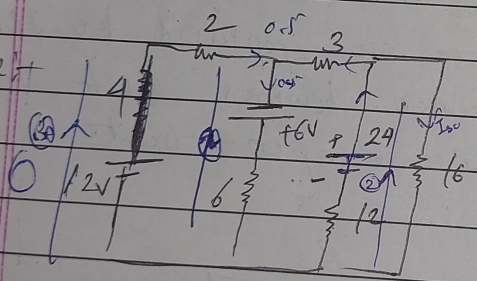

Show that I flowing through resistor 6 is 0.5 A

$$r_n = 4$$


$$I_{sc} = 2.5$$

$$I = \frac{4}{1} \times 1$$

*


Ques

★ Superposition theorem :-

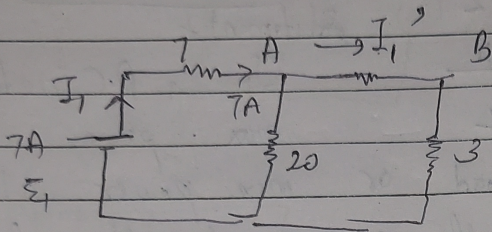

$$I_1' = \frac{7 \times 20}{20 + 3}$$

$$I_1' = 5A \text{ (A to B)}$$

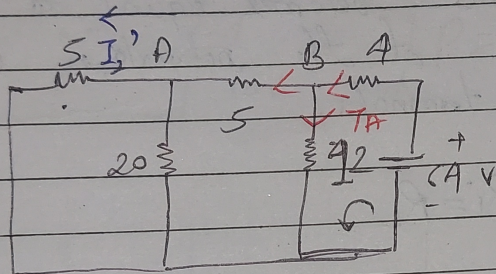


$$I_2 = 7A$$

$$I_2' = \frac{7 \times 12}{12 + 4} = 4A \text{ (B to A)}$$

$$I_2 = 5 - 4A$$

Qv.

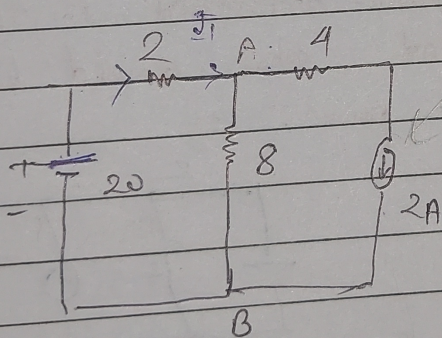


open this circuit?

$$I_1 = 2$$

$$I_2 = 0$$

Soln

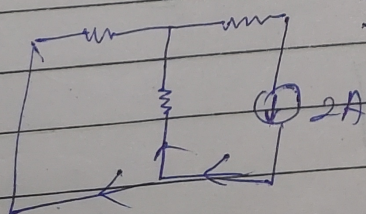

$$I_2 = \frac{2 \times 2}{2 + 8} = \frac{2 \times 2}{10} = 0.4A$$

$$I_0 = I_1 - I_2 = 2 - 0.4 = 1.6A$$

* Max^m Power transfer :- $R_L = R_{TH}$

$$P_{max} = \frac{V_{TH}^2}{4R_L}$$

Statement


In a D.C network, max. power will be consumed by the load or max. power will be transferred from the source to the load, if the load resistance becomes equal to the internal resistance of the network, as viewed from the load terminals.

$$R_{TH} = R_i = R_L$$


Q: A 12 v battery is supplying power to resistive load R_L to as shown in network. Calculate at what value, power transferred to the load will be max. and what would be the value of that max. power.

$$I = \frac{12}{6} = 2A \quad V_{TH} = 2 \times 2 = 4V$$

$$V_{TH} = 4V$$

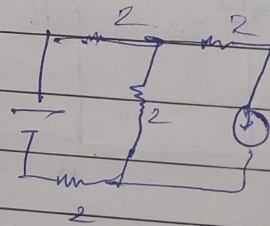

$$P_{TH} = 5.33W = R_i = R_L$$

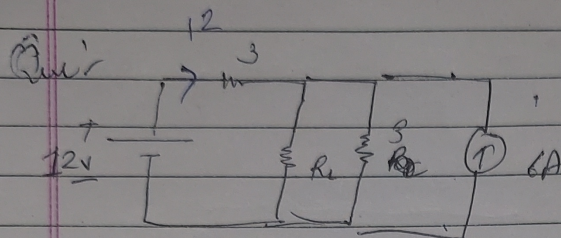


Solⁿ:-

$$I = (2 - 3) = -3$$


$$I_a = 1A$$

$$V_{th} = 15V$$

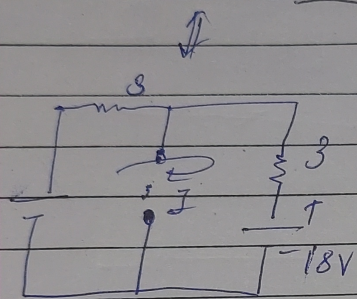

$$P = 37.5W$$

Q.13

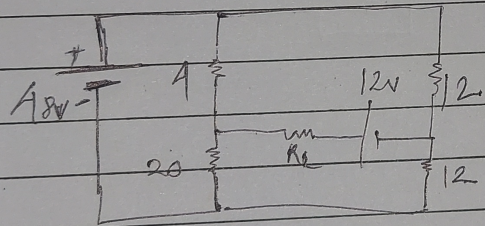

Solⁿ:-

$$V_{th} = 4.4$$

$$R_{th} = 9.33$$

$$P = 0.42W$$